
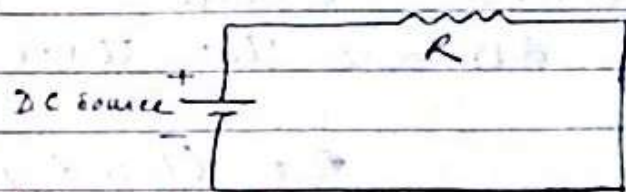


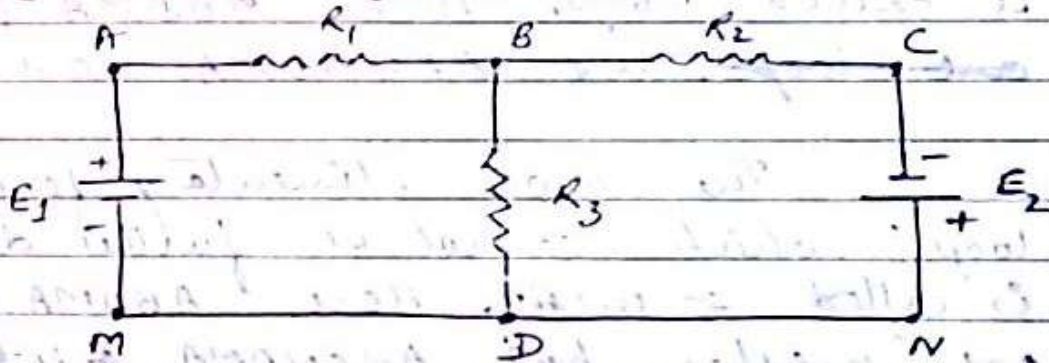DC Network :- The closed path followed by direct current (dc) is called a dc circuit or DC network. The dc circuit essentially consists of a source of dc power (eg. battery, dc generator, etc).



NETWORK TERMINOLOGY



1) Active Element :- The element which supplies energy to the circuit is called active element. E_1 & E_2 are active element in above figure or circuit.

2) Passive Element :- The element which receives energy is called passive element (such as resistor, inductor & capacitor).

3) Node :- It is a point in the network where two or more circuit elements are joined. Eg. A, B, C & D are nodes.

4) Junction - A point in the network where three or more circuit elements are joined is called as junction.

5) Branch - The part of a network which lies between two junction points is called branch. Here DAB , BCD & BD are the three branches.


6) Loop - The closed path of the network is called loop. Here, $ABDMA$ & $BCNDB$ are loops and $ABCNOMA$ are loops.

7) Mesh - The most elementary form of a loop which cannot be further divided is called a mesh. Here, $ABDMA$ & $BCNDB$ are meshes but $ABCNOMA$ is ~~not~~ loop.

CLASSIFICATION OF NETWORK ELEMENTS

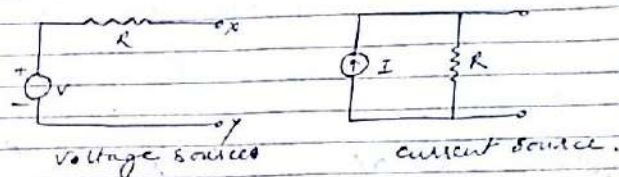- 1) Active Elements
- 2) Passive Elements

Active Elements - The elements which supply energy to the network are called active element. These active elements may be constant voltage sources or constant current sources. Batteries and d.c. generators are normally used as voltage sources while most of the semiconductor devices like transistor etc. are treated as current sources.



2) Passive Elements - The elements which receive energy from the network are called passive elements, such as resistor, inductor & capacitor.

In DC network only resistances are relevant. Inductance & capacitance are relevant only in AC networks.

Resistance - Electrical resistance is the property of a material by virtue of which it opposes the flow of electrons through the material. Unit - Ohm (Ω)

Inductance - Inductance is the property of a material by virtue of which it opposes any change of magnitude or direction of electric current passing through it. Unit - Henry (H)

Capacitance - It is the capability of an element to store electric charge within it. Unit - Farad (F)


Voltage Current Relationship of Network Elements

Network Elements	Voltage (volts)	Currents (amperes)	Power (watts)
$R (\Omega)$	$V = Ri$	$i = \frac{V}{R}$	$P = i^2 R$ $E = i^2 R t$
$L (H)$	$V = L \frac{di}{dt}$	$i = \frac{1}{L} \int V dt$	$P = Li \frac{di}{dt}$ $E = \frac{1}{2} Li^2$
$C (F)$	$V = \frac{1}{C} \int i dt$	$i = C \frac{dV}{dt}$	$P = C V \frac{dV}{dt}$ $E = \frac{1}{2} C V^2$

VOLTAGE SOURCES

A voltage source is a two terminal device whose voltage at any instant of time is independent of the current flowing through its terminals. It maintains the magnitude & wave form of its terminal voltage irrespective of the types of network connected to its terminals. Such type of voltage sources are called ideal voltage sources & such a voltage source must possess zero internal resistance, so that internal voltage drop in the source is zero.

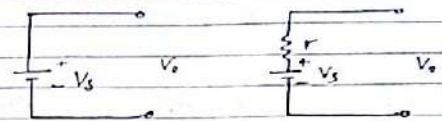In practice none such ideal constant voltage source can be obtained. However, smaller the internal resistance r of a voltage source, closer it comes to an ideal source, etc.



Ideal Voltage Source Practical Voltage Source

Let, battery = $12V = V_s$

Internal resistance = 0.01Ω

When, current is not supplied

$V_o = 12V$ in both the cases.

When current is supplied (say $100A$)


The drop across int. resistance is $1V$

Hence, $V_o = 12V - 1V$ in Practical Voltage source

$V_o = 12V$ in Ideal voltage source

CURRENT SOURCE

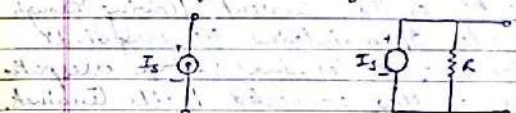An independent ideal current source is a 2 terminal dkt. element that will supply the same current to any load terminated resistance connected across its terminals. The current supplied by the current source is independent of the voltage at the source terminals.



Ideal current source Practical Current source

Examples - photo electric cells used in light meters, motor type gen.


The current source in parallel add algebraically. When current is in the same direction their eqvt. source is sum of two individual sources. If dirⁿ is opp^o eqvt source is diff. of the source value.

INDEPENDENT AND DEPENDENT SOURCE

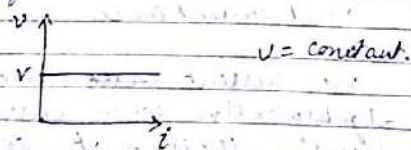- 1) Independent voltage sources :- The independent source is not dependent on any other quantity in the ckt it has a const. value i.e. the strength of a voltage or current is not changed by ~~the source~~ ~~with~~ any variation in the connected n/w. The ~~ind~~ independent sources are of two types: Independent voltage sources & current sources.


The term independent sources ~~indicates~~ indicates that the magnitude of the source is independent of the network to which it is applied & that it exhibits its terminal characteristics even if completely isolated.

Independent voltage source :- An independent voltage source is a two terminal device whose voltage at any instant of time is independent of the current flowing through its terminals. It maintains the magnitude & wave form of its terminal voltage irrespective of the type of N/w connected to its terminals.



The independent voltage source is an ideal source. It does not represent exactly any physical device, because the ideal source could theoretically deliver an infinite amount of energy from its terminals, an automobile storage battery has a terminal voltage of 12V, that remains essentially constant as long as the current drawn from it does not exceed a few amperes.

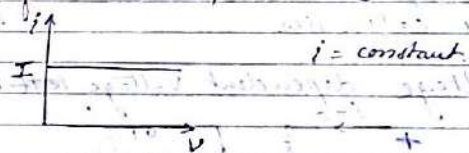Independent current source :- A current source is a two terminal device whose ~~terminal~~ current at any instant of time is independent of the voltage across its terminals. It maintains the magnitude & wave form of its current irrespective of the type of the network connected to its terminals.



Such a source is nonexistence in the real world. However there are some sources which may be very closely approximated to an ideal current source. For eg:- The electron beam of synchrotron operating at ~~different~~ a constant beam current, a pentode vacuum tube amplifier & certain transistor circuit can deliver a constant current to a wide range of loads.


Dependent or Controlled Sources:- It is that source whose magnitude is governed by a current or voltage of the system in which it is situated. In a dependent source the output voltage (or current) depends on another voltage (or current).

In electronic ckt, the current through an element is dependent on a current through some other element or in a MOSFET it is dependent on the voltage across some other elements.

The dependent source is basically a three terminal device. The three terminals are paired, with one common terminal & one pair is referred as input while the other pair as the o/p.

Dependent sources are classified into four categories.


1) Voltage dependent Voltage source.

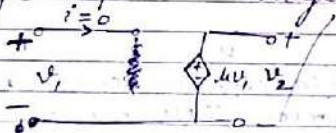


2) Current dependent voltage sources.



3) Current Dependent current source

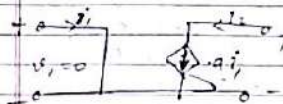

4) Voltage dependent current source.

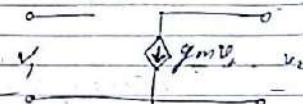

The quantities of input (V_1 & i_1) are controlling quantities whereas the output quantities (V_2 & i_2) are controlled (dependent) quantities. Thus a controlled source is unidirectional in the sense that an input variable controls one of the quantities of the output, whereas the output quantities don't influence the input quantities.

Some physical devices operate almost like ideal dependent source, for eg. an operational ampl^r is a voltage dependent voltage source, a common base transistor is a current dependent current source & a field effect transistor (FET) is a voltage dependent current source.

A dc shunt generator operating at a constant speed and in the linear characteristic of field magnetisation is an example of current dependent voltage source.

Ques 3) A 200Ω resistance is directly p. switched across a 20V battery. What is the current through the resistor? How much is the power loss? Also find the energy consumed in 5 sec.

Solⁿ

$$V = 200 \cdot 20V$$

$$R = 200 \Omega$$


$$I = \frac{V}{R} = \frac{20}{200} = 0.1 \text{ Amp}$$

Power loss, $P = I^2 R = (0.1)^2 \times 200$
 $= 0.01 \times 200$
 $= 2 \text{ watts}$


Energy consumed in 5 sec $= I^2 R t$
 $= 2 \times 5 = 10 \text{ Joules}$

SOURCE CONVERSION

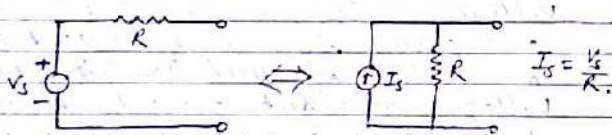A practical voltage source can be converted or transformed to an equivalent practical current source. Similarly, a practical current source can be converted to an equivalent practical voltage source. Replacing of one source by an equivalent source is called a source transformation or source conversion.






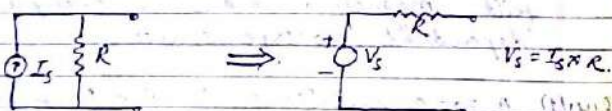Voltage source converted to current source.









Current source converted into voltage source

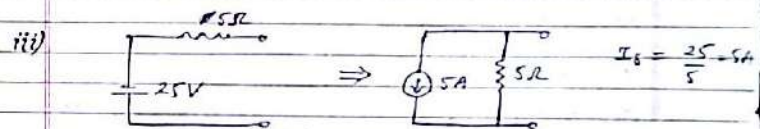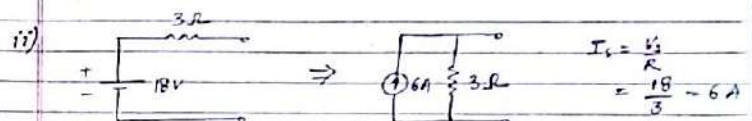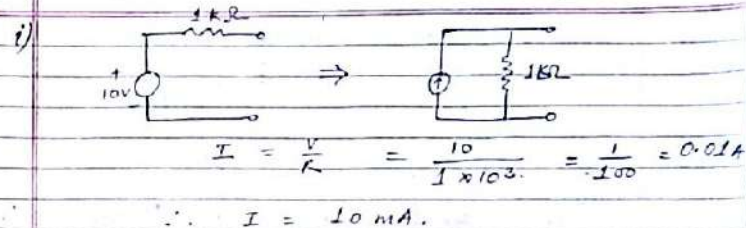Ques 1) Convert the voltage source to a current source.



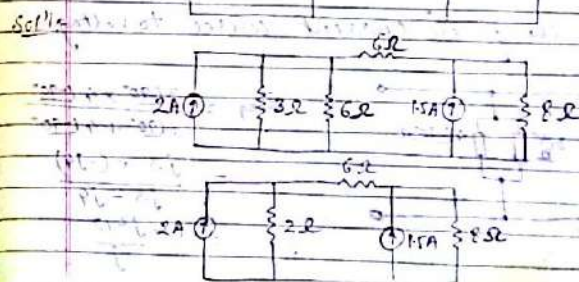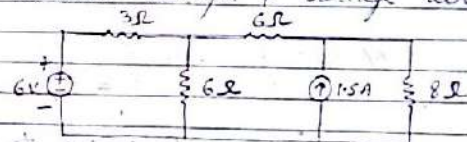Ques In the N/W, use source transformation to determine the current through & voltage across 8Ω resistor.



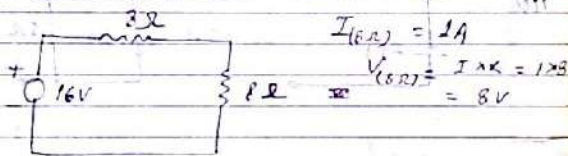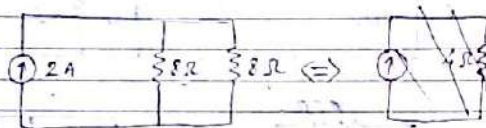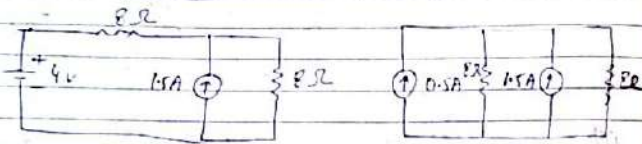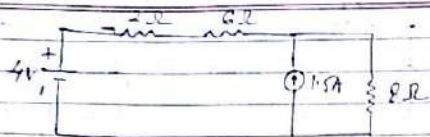


Current through 8Ω resistor, $i = \frac{16}{16} = 1 \text{ amp}$

Voltage across 8Ω resistor

$$V = 8 \times i = 8 \text{ V}$$

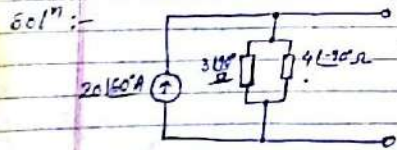Ques: Convert the given current source to voltage source. (For AC)




$$\begin{aligned} Z_{eq} &= \frac{3\angle 90^\circ \times 4\angle -90^\circ}{3\angle 90^\circ + 4\angle -90^\circ} \\ &= \frac{j3 \times (-j4)}{j3 - j4} \\ &= \frac{-j2 \cdot 12}{-j} \end{aligned}$$

$$= \frac{12}{-j} = 12\angle 90^\circ$$

$$Z_{eq} = 12\angle 90^\circ$$

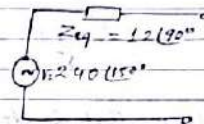
$$V = I \times Z_{eq} = 20\angle 60^\circ \times 12\angle 90^\circ = 240\angle 150^\circ \text{ Volts}$$



Ques: Three resistances of 3, 4 & 5 Ω are connected in parallel and this combination is put in series with 2 Ω resistor.

(a) Find the equl. resistance of the combⁿ (at terminals P & Q)

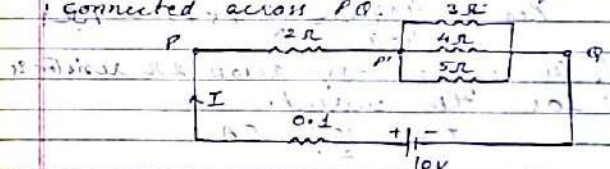(b) Obtain current in each ckt when a battery of 10V with internal resistance of 0.1 Ω is connected across P & Q.



$$\text{Sol}^n: (a) R_{eq}(PQ) = \frac{1}{\frac{1}{3} + \frac{1}{4} + \frac{1}{5}} + 2 = 3.28 \Omega$$

$$(b) I_{in} = \frac{10}{3.28 + 0.1} = 2.96 \text{ A}$$

$$\text{Voltage across } PQ = 10 - 2.96 \times 0.1 = 9.704 \text{ V}$$


$$\text{Drop in } P'Q = 9.704 - 2.96 \times 2 = 3.784 \text{ V}$$

$$I_{(3\Omega)} = \frac{3.784}{3} = 1.26 \text{ A}$$

$$I_{(4\Omega)} = \frac{3.784}{4} = 0.946 \text{ A}$$

$$I_{(5\Omega)} = \frac{3.784}{5} = 0.7568 \text{ A}$$

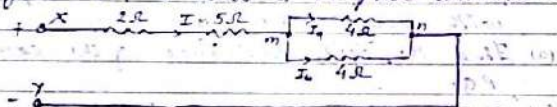Ques Calculate the voltage that is to be connected across terminal x-y in fig. such that the voltage across the 2Ω resistor is 10V . Also find I_a & I_b . What is the power loss in the ckt.



Solⁿ:- \therefore Eqvt. resistance across the terminals x-y.

$$R_{eq} = \frac{4 \times 4 + 5}{4 + 4} = \frac{16}{8} + 5 + 2 = 9\Omega$$

If the voltage drop across 2Ω resistor is 10V , then current.

$$I = \frac{10}{2} = 5\text{A}$$

$$\text{Now Voltage across x-y terminals (V)} = 10 \times 9 = 90\text{V}$$

Voltage across m-n terminals

$$V_{mn} = 90 - 5 \times (2 + 5) = 10\text{V}$$

$$\therefore I_a = \frac{10}{4} = 2.5\text{A}, I_b = \frac{10}{4} = 2.5\text{A}$$

100%

The total power loss in the ckt. is $I^2 R$.
i.e. $5^2 \times 9 = 225\text{W}$.

Kirchoff's laws:-


The law enables easier analysis of an interconnection of any no. of ckt. elements. The Kirchoff's first law deals with flow of current & is popularly known as Kirchoff's current law (KCL) while the second one deals with voltage drop in a closed network and is known as Kirchoff's voltage law (KVL).

1) Kirchoff's current law:- It is a Kirchoff's first law. It states that the algebraic sum of all currents at any node of a circuit is zero.

According to KCL,

$$i_1 + i_2 - i_3 - i_4 - i_5 = 0$$

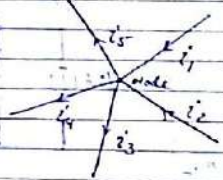
The direction of incoming currents to a node being +ve, the outgoing currents should be taken -ve. \therefore Incoming current & Outgoing current
 \therefore Thus, $i_1 + i_2 = i_3 + i_4 + i_5$



i.e. the algebraic sum of currents entering a node must be equal to the algebraic sum of currents leaving a node.

Ques Find the magnitude & direction of the unknown currents in Fig. Given $i_1 = 10A$, $i_2 = 6A$, $i_5 = 4A$
soln:- $i_1 = i_7 = 10A$

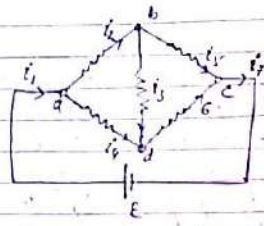
At node a,
 $i_1 = i_2 + i_4$
 $i_4 = i_1 - i_2$
 $= 10 - 6 = 4A$



At node b,
 $i_2 = i_3 + i_5$
 $i_3 = i_2 - i_5$
 $= 6 - 4 = 2A$

At node c,
 $i_7 = i_5 + i_6$
 $i_6 = i_7 - i_5$
 $= 10 - 4 = 6A$

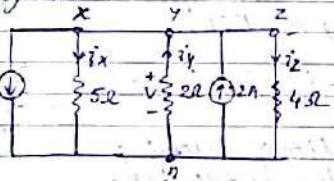Ques Find V_x and the magnitude & direction of the unknown currents in the branches x, y, z .
soln:-



Let the unknown currents in branches x, y, z be i_x, i_y & i_z resp. & their dirⁿ shown in fig.

At node y, Applying KCL,
 $10 + i_x + i_z = i_y + 2$
 $i_x + i_z - i_y = (-8) \quad \text{--- (i)}$

Now by Ohm's law,
 $i_x = \frac{V}{5} A$, $i_y = -\frac{V}{2} A$ & $i_z = \frac{V}{4} A$

Now putting these values in equ (i) we get

$$\frac{V}{5} + \frac{V}{2} + \frac{V}{4} = -8$$

$$\frac{4V + 10V + 5V}{20} = -8$$

$$-V = -160$$

$$V = -160 \text{ Volts}$$

$$V = -8.42 \text{ Volts}$$

-ve sign indicates that node n to be +ve & at higher potential.

$$V = -8.42 \text{ Volts}$$

$$i_x = \frac{-8.42}{5} = -1.684 A$$

$$i_y = -\left(\frac{-8.42}{2}\right) = 4.21 A$$


$$i_z = \frac{-8.42}{4} = -2.1 A$$

Dirⁿ of currents


$$i_x = n \text{ to } x$$

$$i_y = n \text{ to } y$$

$$i_z = n \text{ to } z$$

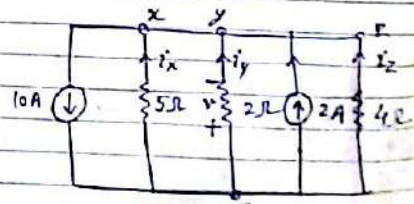

Ques Find i_1 & i_2

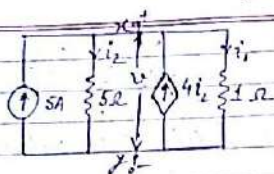

Solⁿ:- Applying KCL at x.

$$i_2 + i_1 = 5 + 4i_2$$

$$i_1 - 3i_2 = 5 \quad \text{--- (1)}$$

Also, $i_2 = \frac{V}{5} \text{ A}$ & $i_1 = \frac{V}{1} \text{ A}$

Putting in eqn (1).

$$-3 \frac{V}{5} + V = 5$$

$$-3V + 5V = 25$$

$$2V = 25$$



$$V = 12.5 \text{ V}$$

$$i_1 = 12.5 \text{ A}$$

$$i_2 = \frac{12.5}{5} = 2.5 \text{ A}$$

Kirchoff's Voltage Law (KVL)

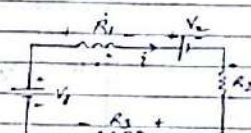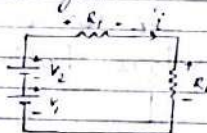The algebraic sum of voltages (or voltage drops) in any closed path of network that is traversed in a single direction is zero.



$$i(R_1 + R_2) = V_1 + V_2$$

$$i(R_1 + R_2) = V_1 + V_2$$


$$i = \frac{V_1 + V_2}{(R_1 + R_2)}$$

$$-V_1 + iR_1 + V_2 + iR_2 + iR_3 = 0$$

$$i(R_1 + R_2 + R_3) + V_2 = V_1$$

$$i = \frac{V_1 - V_2}{(R_1 + R_2 + R_3)}$$

Ques Find current i in fig.

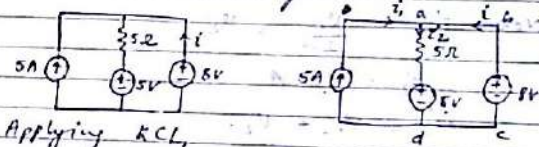

Solⁿ:- Applying KCL,

$$5 - i_2 = i_1 + i$$

$$i_2 = 5 + i$$

KVL in loop abcd.

$$5i_2 + 5 = -8$$

$$i_2 = \frac{3}{5} \text{ A}$$

Using eqn (1) & (2) we get

$$i = 5 + \frac{3}{5} = \frac{28}{5} = 5.6 \text{ A}$$

$$5 + \frac{3}{5} - 5 = i \Rightarrow i = \frac{3}{5} = 0.6 \text{ A}$$

$$T_1 = \frac{\Delta_1}{\Delta} \quad T_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} 12 & -1 \\ -6 & 4 \end{vmatrix}, \Delta_2 = \begin{vmatrix} 3 & 12 \\ -1 & -6 \end{vmatrix} \cdot 4$$

$$\Delta = \begin{vmatrix} 3 & -1 \\ -1 & 4 \end{vmatrix}$$

$$\Delta_1 = 42, \Delta_2 = -6, \Delta = 11$$

$$i_1 = \frac{42}{11}, i = 3.81$$

$$i_2 = \frac{4 - 6}{11} = -0.54$$


$$I_1 = 3.81 \text{ A}$$

$$I_3 = I_1 - I_2$$

$$I_2 = -0.54 \text{ A}$$

$$= 3.81 + 0.54$$

$$= 4.35 \text{ A}$$

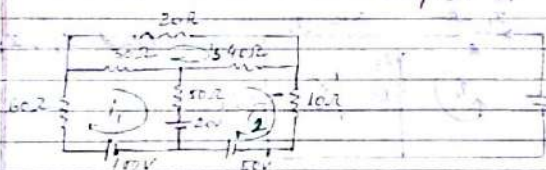

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix}$$

$$\begin{bmatrix} 140 & -50 & -30 \\ -50 & 100 & -40 \\ -30 & -40 & 90 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 80 \\ 70 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 140 & -50 & -30 \\ -50 & 100 & -40 \\ -30 & -40 & 90 \end{vmatrix} = 140(9000 - 1600) + 50(-4500 - 1200) + 30(2800 + 3600)$$

$$= 140 \times 7400 + 50 \times 6700 + 30 \times 5000$$

$$= 1036000 + 335000 + 150000$$

$$\Delta = 1521000$$

$$\Delta_1 = \begin{vmatrix} 80 & -50 & -30 \\ 70 & 100 & -40 \\ 0 & -40 & 90 \end{vmatrix} = 80(9000 - 1600) + 50(6300) + 30(2800)$$

$$= 80 \times 7400 + 50 \times 6500 + 30 \times 2800$$

$$= 592000 + 315000 + 84000$$

$$= 723000$$

$$i = \frac{\Delta_1}{\Delta} = \frac{723000}{1521000} = 0.475$$

$$i = \frac{12}{25} = 0.48$$

$$i = \frac{12}{25} = 0.48$$

$$i = \frac{12}{25} = 0.48$$


$$i = \frac{12}{25} = 0.48$$

$$i = \frac{12}{25} = 0.48$$

$$i = \frac{12}{25} = 0.48$$

$$i = \frac{12}{25} = 0.48$$

WIRE VOLTAGE METHOD

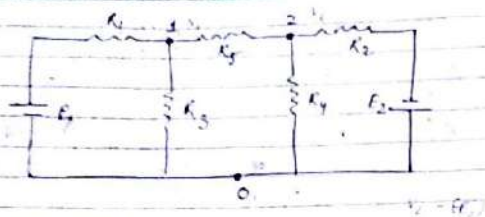

MCQs - Node 1

$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_3} = 0$$

ACL of Node 2,

$$\frac{V_2 + I_2}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2}{R_4} = 0$$

Refracting.

$$\frac{V_1}{R_1} + \frac{V_1}{R_5} + \frac{V_1}{R_3} - \frac{V_2}{R_5} - \frac{E_1}{R_1} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5}\right) V_1 - \frac{1}{R_5} V_2 = \frac{E_1}{R_1}$$

$$(G_1 + G_3 + G_5) V_1 - G_5 V_2 = G_1 E_1 \quad \text{--- (1)}$$

$$\left(\frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_4} \right) R_2 V_2 - \frac{V_1}{R_5} = -\frac{E_2}{R_2}$$

$$(G_2 + G_4 + G_5)V_2 - G_5V_1 = -G_2E_2 \quad \text{--- (2)}$$

$$i_1 = G \frac{E_1}{R_1} = G_1 E_1$$

$$i_L = \frac{E_L}{R_L} - G_2 E_2$$

classmate

144

Figure 1

classmate

2004

Stacy

Equations: Equations (1) & (2) can be written in matrix form as

$$\begin{bmatrix} G_1 + G_3 + G_5 & -G_5 \\ -G_5 & G_2 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} G_1 E_1 \\ -G_1 E_2 \end{bmatrix}$$

$$\begin{bmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 I_1 \\ 2 I_2 \end{bmatrix}$$

where,

$G_{ii} \rightarrow$ sum of all conductances connected at node i


$G_2 \rightarrow \text{---} \parallel \text{---} Z$

$G_{12} = G_{21} \rightarrow$ Sum of all conductance connected b/w node 1 & 2
 $\Sigma I_i \rightarrow$ Algebraic sum of all currents sources
 connected at a the free node 1

$\Sigma T \rightarrow$ _____ // _____ node 2

Similarly, for 3 nodes we have
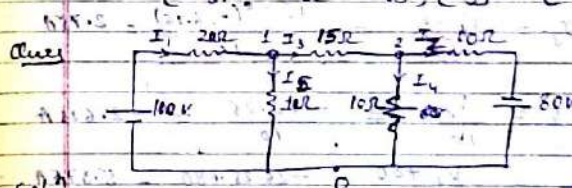
$$\begin{bmatrix} G_{11} & -G_{12} & -G_{21} \\ -G_{21} & G_{22} & -G_{23} \\ -G_{31} & -G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \Sigma I_1 \\ \Sigma I_2 \\ \Sigma I_3 \end{bmatrix}$$



Quay

5072

$$\begin{bmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \sum I_1 \\ \sum I_2 \end{bmatrix}$$

$$G_{11} = \frac{1}{20} + \frac{1}{10} + \frac{1}{15} = \frac{65}{300} = \frac{13}{60}$$

$$G_{22} = \frac{1}{15} + \frac{1}{10} + \frac{1}{10} = \frac{40}{150} = \frac{4}{15}$$

$$G_{12} = G_{21} = \frac{1}{15}$$

$$\sum I_s = \frac{100}{20} = 5 \text{ A}$$

$$\sum I_o = -\frac{80}{10} = -8 \text{ A}$$

$$\begin{bmatrix} \frac{13}{60} & \frac{1}{15} \\ \frac{1}{15} & \frac{4}{15} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ -8 \end{bmatrix}$$

or solving matrix

$$V_1 = 15 \text{ V} \quad V_2 = -26.25 \text{ V}$$

$$I_1 = \frac{100 - V_1}{20} = \frac{100 - 15}{20} = 4.25 \text{ A}$$


$$I_5 = \frac{V_1}{10} = \frac{15}{10} = 1.5 \text{ A}$$

$$I_3 = \frac{V_1 - V_2}{15} = \frac{15 - (-26.25)}{15} = 2.75 \text{ A}$$

$$I_4 = \frac{V_2}{10} = \frac{-26.25}{10} = -2.625 \text{ A}$$

$$I_2 = \frac{V_2 + 80}{10} = \frac{-26.25 + 80}{10} = 5.375 \text{ A}$$

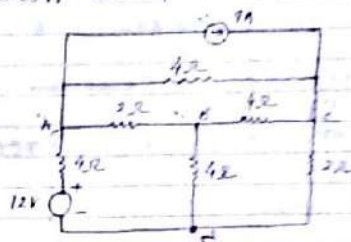Ques Use nodal analysis to determine the voltage across BC & the current in the 12V source.



At node A,

$$\frac{V_1 - 12}{4} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} + 9 = 0$$

$$-V_2 + V_1 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) - \frac{V_3}{2} + 9 - \frac{12}{4} = 0$$

$$-V_2 + 2V_1 - \frac{V_3}{2} = -\frac{33}{2} \quad \text{--- (1)}$$

$$-V_3 + 4V_1 - 2V_2 - 24 = 0$$

$$0 = 4V_1 - 2V_2 - V_3 = -24 \quad \text{--- (2)}$$

At node B,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 - V_3}{4} = 0$$

$$V_2 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{4} \right) - \frac{V_1}{2} - \frac{V_3}{4} = 0$$

$$V_2 - \frac{V_1}{2} - \frac{V_3}{4} = 0$$

$$4V_2 - 2V_1 - V_3 = 0$$

$$+2V_1 - 4V_2 + V_3 = 0 \quad \text{--- (3)}$$

At node C,

$$\frac{V_3 - V_2}{4} + \frac{V_3 - V_1}{4} + \frac{V_3}{2} - 9 = 0$$

$$V_3 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) - \frac{V_2}{4} - \frac{V_1}{4} + 18 - 9 = 0$$

$$V_3 - \frac{V_2}{4} - \frac{V_1}{4} + 9 = 0 \quad \text{--- (3)}$$

$$4V_3 - V_2 - V_1 + 36 = 0 \quad \text{--- (3)}$$

$$V_1 + V_2 - 4V_3 = 36 \quad \text{--- (3)}$$



$$4V_1 - 2V_2 - V_3 = -24$$

$$2V_1 - 4V_2 + V_3 = 0$$

$$6V_1 - 6V_2 = -24$$

$$V_1 - V_2 = -4 \quad \text{--- (4)}$$

multiply eqn (3) by 4, we get.

$$8V_1 - 16V_2 + 4V_3 = 0$$

Now add. with

$$V_1 + V_2 - 4V_3 = -12$$

$$9V_1 - 15V_2 = -12$$

$$3V_1 - 5V_2 = -4 \quad \text{--- (5)}$$

eqn (4) x 3 =

$$3V_1 - 3V_2 = -12$$

$$3V_1 - 5V_2 = -4$$

$$2V_2 = -8$$

$$V_2 = -4 \text{ V}$$

$$V_1 + 4 = -4$$

$$V_1 = -8$$


$$V_3 = -8 - 4 - 4V_3 = 1 - 12$$

$$-4V_3 = 0$$

$$V_3 = 0$$

Voltage across BC = $V_2 - V_3$
 $V_{BC} = -4 \text{ V}$

Current in 12V source = $V_1 - 12$

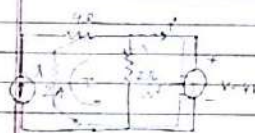

$$= -8 - 12$$

$$= -20 \text{ V}$$

$$= -5 \text{ A}$$

Thévenin's Theorem

Statement → Any two terminal bilateral linear dc circuit can be replaced by an equivalent circuit consisting of a voltage source & a series resistor.

Let, a simple dc ckt. we are to find I_L by Thévenin's theorem.



Steps

- 1) Remove the load resistor R_L & find the open ckt. voltage

- 2) (V_{OC}) across the open circuited load terminals by formula


$$V_{OC} = I R_3$$

$$= \frac{V_S}{R_1 + R_3} \times R_3$$

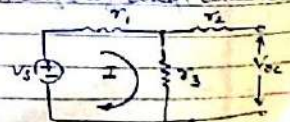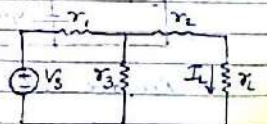

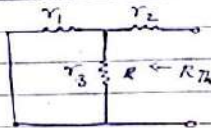
- 2) Deactivate the constant sources & find the internal resistance of or the venous resistance of the source side looking through the open ckt load terminals.

$$R_{Th} = r_2 + \frac{r_1 r_3}{r_1 + r_3}$$



- 3) Obtain Thevenin's Equivalent ckt by placing R_{Th} in series with V_{oc}

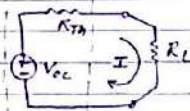
- 4) Reconnect R_L across the load terminals.



Now,
Load Current

$$I_L = \frac{V_{oc}}{R_{Th} + R_L} \text{ Amp.}$$

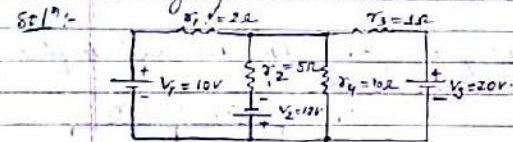
Ques Find the current through the 10Ω resistor utilizing Thevenin's Theorem.



Remove the load resistor $r_4 = 10\Omega$.

is CL At Node C,

$$I_1 + I_3 - I_2 = 0$$

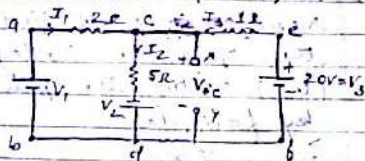

$$\frac{V_1 - V_{oc}}{2} + \frac{V_2 - V_{oc}}{1} - \frac{V_{oc} + V_2}{5} = 0$$

$$\frac{10 - V_{oc}}{2} + \frac{20 - V_{oc}}{1} - \frac{V_{oc} + 20}{5} = 0$$

$$-V_{oc} \left(\frac{1}{2} + 1 + \frac{1}{5} \right) + \frac{10}{2} + 20 - \frac{12}{5} = 0$$

$$-V_{oc} \left(\frac{5+10+2}{10} \right) + \frac{20+10-12}{10} = 0$$


$$-V_{oc} \times \frac{17}{10} + \frac{18}{10} = 0$$

$$-V_{oc} = \frac{-18}{17} \times \frac{10}{10} = \frac{-2.2}{17}$$

$$V_{oc} = 13.29 \text{ V}$$

Now, Remove voltage source by short ckt.

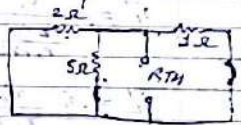
$$R_{Th} = \frac{1}{\frac{1}{2} + \frac{1}{5} + \frac{1}{1}} = \frac{10}{17} \Omega$$



Thevenin's Eqvt Ckt.

$$I_4 = \frac{V_{oc}}{R_{Th} + r_4}$$

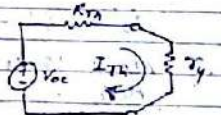
$$I_4 = \frac{13.29}{\frac{10}{17} + 10} = 1.26 \text{ A}$$



Superposition Theorem

Statement :- If a no. of voltage or current sources are acting simultaneously in a linear network, the resultant current in any branch is the algebraic sum of the currents that would be produced in it when each source acts alone, replacing all other independent sources by their internal resistances.

Let the ckt.

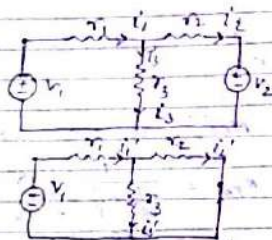

V_2 is s/c

Then,

$$i_1' = \frac{V_1}{R_1 + R_3}$$

$$i_2' = i_1' \cdot \frac{R_3}{R_2 + R_3}$$

$$i_3' = i_1' - i_2'$$

Now, V_1 is shorted.

Here,

$$i_2'' = \frac{V_2}{\frac{R_1 R_3}{R_1 + R_3} + R_2}$$

$$i_1'' = i_2'' \cdot \frac{R_2}{R_2 + R_3} \quad \& \quad i_3'' = i_2'' - i_1''$$

According to superposition theorem,

$$i_3 = i_3' + i_3''$$


$$i_2 = i_2' - i_2''$$

$$i_1 = i_1' - i_1''$$

Steps :-

- 1) Take only one independent source of voltage / current and deactivate the other independent voltage / current sources (for voltage sources, remove the source and short the respective ckt terminals & for current sources, just delete the source keeping the respective ckt terminals open). Obtain branch currents.
- 2) Repeat the above step for each of the independent sources.
- 3) To determine the net branch current applying superposition theorem, just add the currents obtained in step 1 & step 2 for each branch.

Ques Find current through 5Ω resistor.

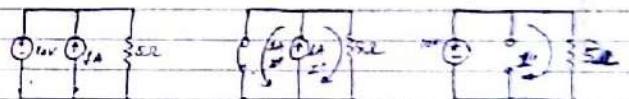


Soln:- Case 1, Voltage source is s/c (deactivating V_s)
Current in 5Ω resistor is zero
 $I' = 0$

Case 2, Deactivating current source (o/c current source)
Current in 5Ω resistor, $I'' = \frac{10}{5} = 2A$

By principle of superposition
 $I = I' + I''$

Current in 5Ω resistor, $I = 2A$.

Ques

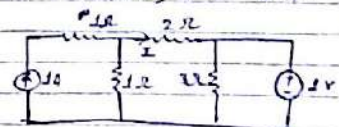

Find I !