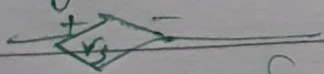


Dependent


- i) Depends on some other circuit quantity which may either be voltage or current
- ii) Parts of models used to represent electrical properties of electronic devices such as operational amplifiers, transistors etc
- iii) Required 4 terminals
a pair for control
Other pair shows properties of source

- iv) 4 types
 - Vol dep Vol so
 - Vol dep Cur so
 - Cur dep Vol so
 - Cur dep Cur so

- v) Dep Vol so produces Vol as func of Vol elsewhere in given cir



- vi) Dep Cur --- func of Cur ---

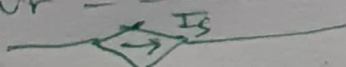

Independent


- i) independent does not depend on any other quantity in circuit

- ii) Actually exist as physical entities like DC generator, alternator, accumulator etc.

- iii) only two terminals

- 2 types
 - indep Vol so
 - indep Cur so

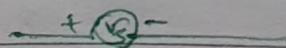
- v) Ideal
Indep Vol so maintains specified Vol over the insep of Cur drawn thru it



- Total indep Cur so --- specified Cur --- regardless of Vol acc term ---



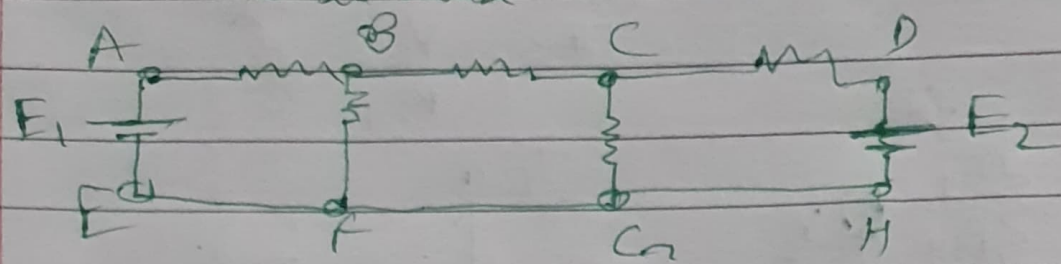Node → A pt where two or more ^{elements join together} branches meet
called node



A, B, C, D are nodes

Junction where three or more branches meet
→ Every jn is a node but not every node is jn
→ B, C are jn
→ current is divided.

Active element

→ element which supplies energy to circuit is active
→ E_1, E_2 are active
→ imp in circuit cuz provide necessary energy to other circuit components to work.

Passive element

→ receives energy is passive which it either absorbs or ^{or dissipates}
→ resistor, inductor capacitor
→ R_1, R_2, R_3, R_4, R_5 are passive
→ also called parameters of network

KCL

→ States total current flowing towards a jn pt is equal to tot cur flowing out of jn pt.

or

Algebraic sum of all the cur meeting at a jn pt is always zero

→ App → Nodal analysis

→ Math exp $\sum I = 0$


Open circuit

→ Sign conv

i) Current flowing towards = +ve

ii) " " away from jn pt = -ve

Eg

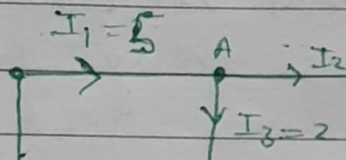

KCL

at node A

$$I_1 = I_2 + I_3$$

$$5 = I_2 + 2$$

$$\boxed{I_2 = 3 \text{ A}}$$

KVL

In any network, the alg sum of voltage ^{drop} across circuit elements in ^{closed} loop is equal to alg sum of emf across closed loop.

or

The alg sum of all branch voltages across a closed loop is always zero.

Math $\sum V + IR = 0$
 $\sum V = 0$

App Mesh / loop analysis

Sign

→ When cur flows thro resis, the voltage drop occurs across resis, the polarity of voltage drop always depends on direction of cur. Cur flows from higher pot. to lower pot.

$\xrightarrow{I_1} R_1 \rightarrow$
 $V = -I_1 R_1$

→ Pot rise - ~~cur~~ travelling from negative to positively marked terminal must be considered +ve

$\xrightarrow{I_2} E_2 \rightarrow$

$V = +E_2$


→ Pot drop - travelling from +ve to -ve marked terminal must be considered -ve

$\xrightarrow{I_3} E_3 \rightarrow$

$V = -E_3$

eg →

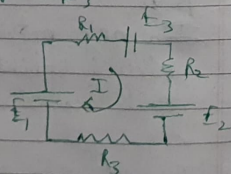$\sum V = +E_1 - IR_1 - E_3 - IR_2$
 $-E_2 - IR_3$
 $= 0$



Mesh analysis

* When no. of branches in a network ~~is~~, then using conventional methods for the analysis of network can lead to complications

∴ To simplify the soln of such networks, the method of mesh / loop analysis is used.

* It is an app of KVL which states that if sum of all branch voltages in closed loop is 0 i.e. $\sum V = 0$.


∴ ~~expansion~~ ~~steps~~ for mesh analysis :-

- Find no. of meshes, convert all current source to equivalent voltage source.
- Assign mesh current to each mesh assuming flow of cur to be clockwise.
- Apply KVL in each mesh and write eqn.
- no. of eqn will be no. of unknown mesh currents.
- solve eqn to find unknown mesh cur.

* Sign conven

→ (Same as KVL) -

*

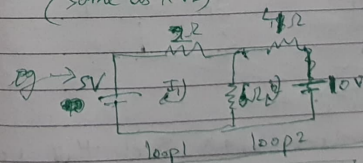

Loop 1, $90 - 9I_1 - 6(I_1 - I_2) = 0$
 $90 - 9I_1 - 6I_1 + 6I_2 = 0$
 $15I_1 - 6I_2 = 90$
 $5I_1 - 2I_2 = 30$ (1)

Loop 2, $-6(I_2 - I_1) - 2I_2 - 40 = 0$
 $-6I_2 + 6I_1 - 2I_2 - 40 = 0$
 $6I_1 - 8I_2 = 40$
 $3I_1 - 4I_2 = 20$ (2)


$I_1 =$

Nodal Analysis

- * App of KCL which states that cur flow ^{towards a jn pt} into node is equal to tot cur flow out of jn pt.
- * In this method, one of the nodes is taken as reference node or zero pot node or datum node whose pot is 0 & ~~assumed~~ and the pot diff b/w each of the other & reference node is expressed in terms of unknown voltage (V_A, V_B, \dots)
- * Then KCL is applied at each node assuming the possible direction of branch current.
- * Node vol then reduces no. of eqⁿ to be solved to find unknown quantities.
- * If there are (n) no. of nodes then there will be (n-1) no. of nodal eqⁿ in terms of (n-1) no. of unknown ~~nodal~~ nodal voltages.

Sign convⁿ

Explanation:

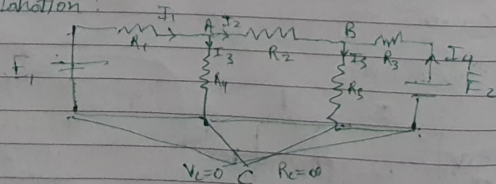

Consider circuit of three nodes such that node C is taken as reference node & V_A, V_B be voltages at

node A & B w.r.t ref node C

Apply KCL at node A, $-I_1 = I_2 + I_3$

$$\frac{E_1 - V_A}{R_1} = \frac{V_A - V_B}{R_2} + \frac{V_A}{R_4} \quad (1)$$

at node B, $I_5 = I_2 + I_4$

$$\frac{V_B}{R_5} = \frac{V_A - V_B}{R_2} + \frac{E_2 - V_B}{R_3} \quad (2)$$

In this way we can find values of V_A & V_B by the help of above two eqⁿs.

Energy Sources

Two types further 2 types

Nol

Ideal


Cur

Prax

Ideal Vol So

defined as which

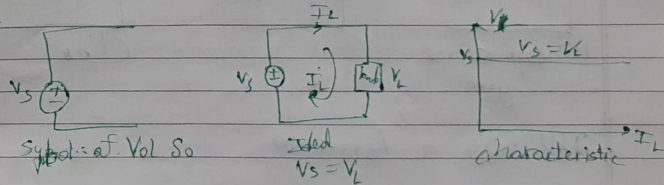gives const voltage across its terminal irrespective of the current drawn ~~by~~ thru terminal





Internal resistance = 0
[R_{sp} = 0]

c) Pract Vol So

Every vol so has small int res in series with vol so & rep as R_{se}


Due to R_{se} , vol across terminals decrease slightly with int in cur & is given by exp

$$V_L = V_S - I_L R_{se}$$

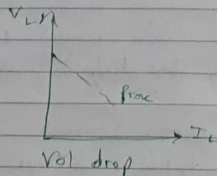
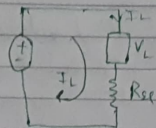


→ Ideal cur source

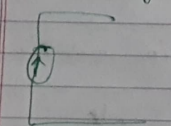as which gives const current thro its terminal irres of voltage appearing across its terminal.



DC cur source
Sym

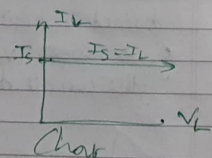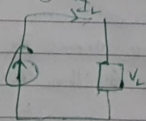



Int Resis = $R_{SH} = \infty$

Pract Cur So

Every cur so have int Resis connected parallel to cur so given by R_{SH}


Due to R_{SH} current ~~across~~ ^{thru} terminal decreases slightly as voltage increases

$$i.e. I_L = I_S - \frac{V_L}{R_{SH}}$$

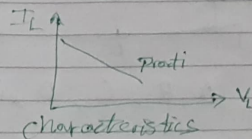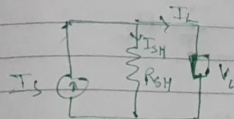


Source transformation / Conversion

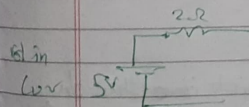
- technique to convert one kind of source into other with resis in series
- Voltage So can be conv into equivalent cur so with resis in parallel
- Cur so --- resis parallel --- Vol so --- resis series



Vol in
Cur

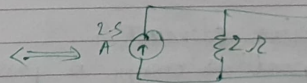

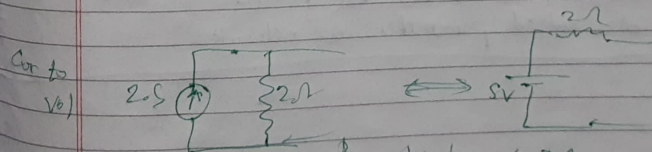By ohm's $I = \frac{V}{R} = \frac{5}{2} = 2.5 \text{ A}$



Cur to
Vol

By ohm's $V = IR$
 $V = 2.5(2) = 5 \text{ V}$


$$P_T = \frac{1}{2} \left[\frac{1}{4} - \frac{x}{20} \cos 2x \right]$$

$$= \frac{1}{2} \left[\frac{1}{4} - \frac{x}{2} \sin 2x \right]$$

$$P_T = \frac{1}{8} - \frac{x}{8} \sin 2x$$

$$\left[y = C_1 \cos 2x + C_2 \sin 2x + \frac{1}{8} - \frac{x}{8} \sin 2x \right]$$

Q9) Current thru 5Ω loop analysis

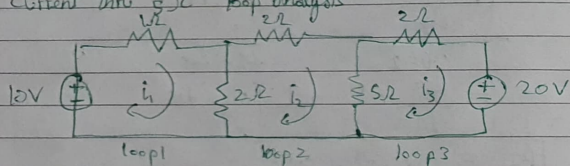

$$\begin{aligned} \text{KVL in loop ①, } 10 - i_1 - 2(i_1 - i_2) &= 0 \\ 10 - i_1 - 2i_1 + 2i_2 &= 0 \\ -3i_1 + 2i_2 + 10 &= 0 \\ \boxed{3i_1 - 2i_2 = 10} \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{KVL in loop ②, } -2(i_2 - i_1) - 2i_2 - 5(i_2 - i_3) &= 0 \\ -2i_2 + 2i_1 - 2i_2 - 5i_2 + 5i_3 &= 0 \\ 2i_1 - 9i_2 + 5i_3 &= 0 \quad \text{--- (2)} \\ \boxed{2i_1 + 5i_3 = 9i_2} \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} \text{KVL in loop ③, } -20 - 5(i_3 - i_2) - 2i_3 &= 0 \\ -5i_3 + 5i_2 - 2i_3 &= 20 \\ \boxed{5i_2 - 7i_3 = 20} \quad \text{--- (3)} \end{aligned}$$

$$\begin{aligned} 15i_1 - 10i_2 &= 100 \\ +10i_2 - 14i_3 &= 40 \\ 15i_1 - 14i_3 &= 90 \end{aligned}$$

$$3i_1 + 3i_2 - 7i_3 = 30$$

$$\text{eq (1), } i_1 = \frac{10 + 2i_2}{3}$$

$$\text{eq (3), } i_3 = \frac{5i_2 - 20}{7}$$

$$2 \left(\frac{10 + 2i_2}{3} \right) - 9i_2 + 5 \left(\frac{5i_2 - 20}{7} \right) = 0$$

$$\frac{20 + 4i_2}{3} - 9i_2 + \frac{25i_2 - 100}{7} = 0$$

$$\frac{140 + 28i_2 - 189i_2 + 75i_2 - 300}{21} = 0$$

$$-160 - 86i_2 = 0$$

$$i_2 = \frac{-160}{86}$$


$$\boxed{i_2 = -1.86 \text{ A}}$$

$$i_1 = \frac{10 + 2(-1.86)}{3} = \frac{10 - 3.72}{3} = \frac{6.28}{3} = 2.09 \text{ A}$$

$$i_3 = \frac{5(-1.86) - 20}{7} = \frac{-9.3 - 20}{7} = \frac{-29.3}{7} = -4.18 \text{ A}$$

$$\begin{aligned} \text{Current thru } 5\Omega &= -5(i_3 - i_2) \\ &= i_2 - i_3 \\ &= -1.86 + 4.18 \\ &= 2.32 \text{ A} \end{aligned}$$

10>

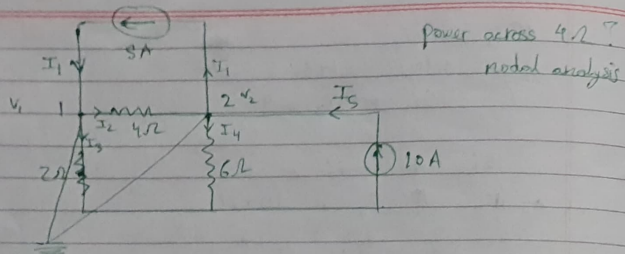

power across 4Ω ?
nodal analysis

KCL at Node 1, $I_1 = I_2 + I_3$

$$5 = \frac{V_1 - V_2}{4} + \frac{V_1}{2}$$

$$5 = \frac{V_1 - V_2 + 2V_1}{4}$$

$$20 = 3V_1 - V_2$$

$$V_2 = 3V_1 - 20 \quad (1)$$

KCL at Node 2, $I_5 + I_2 = I_4 + I_1$

$$10 + \frac{V_1 - V_2}{4} = \frac{V_2}{6} + 5$$

$$5 = \frac{V_2 - (V_1 - V_2)}{4}$$

$$5 = \frac{4V_2 - 6V_1 + 6V_2}{24}$$

$$120 = 10V_2 - 6V_1$$

$$60 = 5V_2 - 3V_1$$

$$60 = 5(3V_1 - 20) - 3V_1$$

$$60 = 15V_1 - 100 - 3V_1$$

$$160 = 12V_1$$

$$V_1 = 13.33 \text{ volt}$$

$$V_2 = 3(13.33) - 20$$

$$= 39.99 - 20$$

$$V_2 = 19.99 \text{ volt}$$

Current thro $4\Omega = I_2 = \frac{V_1 - V_2}{4} = \frac{13.33 - 19.99}{4}$

$$= \frac{-6.66}{4}$$


$$= -1.665 \text{ A}$$

Power thro $4\Omega = I^2 R$


$$= (-1.665)^2 \times 4$$

$$= 2.772 \times 4$$

$$= 11.0889 \text{ watt}$$

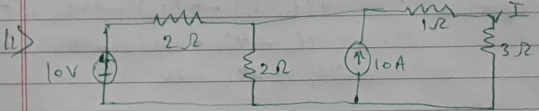



Current I ?
node voltage method

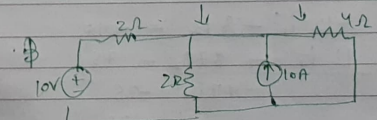

$$V = IR$$

$$V = 10(2)$$

$$V = 20 \text{ V}$$

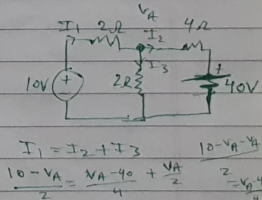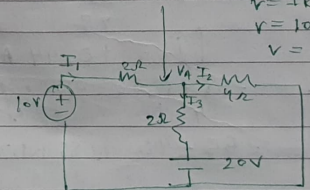

KCL at A, $I_1 = I_2 + I_3$

$$\frac{10 - V_A}{2} = \frac{V_A}{4} + \frac{V_A - 20}{2}$$

$$\frac{10 - V_A}{2} = \frac{2V_A + 2V_A - 40}{4}$$


$$20 - 2V_A = 3V_A - 40$$

$$60 = 5V_A$$

$$I = I_2 = \frac{V_A}{4} = \frac{12}{4} = 3 \text{ A}$$

9.46, 0.44

12

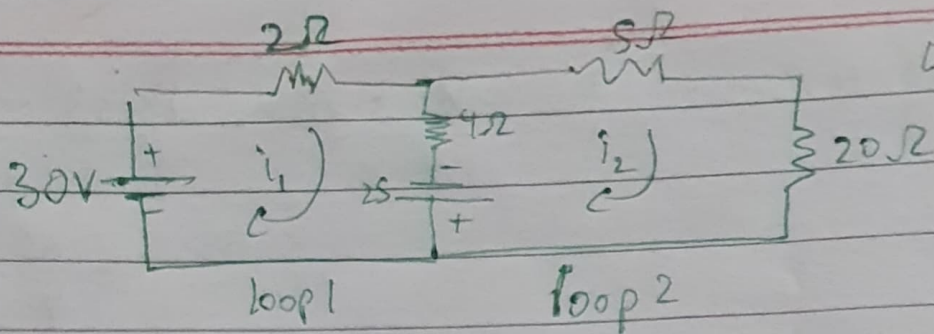

Current thru $5\Omega = ?$

mesh analysis

KVL in loop 1, $30 - 2i_1 - 4(i_1 - i_2) + 25 = 0$
 $30 - 2i_1 - 4i_1 + 4i_2 + 25 = 0$
 $-6i_1 + 4i_2 = -55 \quad \text{--- (1)}$

KVL loop 2, $-25 - 4(i_2 - i_1) - 5(i_2) - 20i_2 = 0$
 $-25 - 4i_2 + 4i_1 - 25i_2 = 0$
 $4i_1 - 29i_2 = 25$

$$-12i_1 + 8i_2 = -110$$

$$12i_1 - 87i_2 = 75$$

$$-79i_2 = -35$$

$$i_2 = + \frac{35}{79}$$

$$i_2 = +0.44 \text{ A}$$

Eq (1), $i_1 = \frac{-55 + 6i_2}{4} = \frac{-55 + 2.65}{4} = \frac{-52.35}{4}$

$$i_1 = \frac{+55 + 4i_2}{6} = \frac{55 + 1.76}{6} = \frac{56.76}{6}$$

Current thru $5\Omega = i_2 = 0.44 \text{ A}$

$$i_1 = 9.46 \text{ A}$$